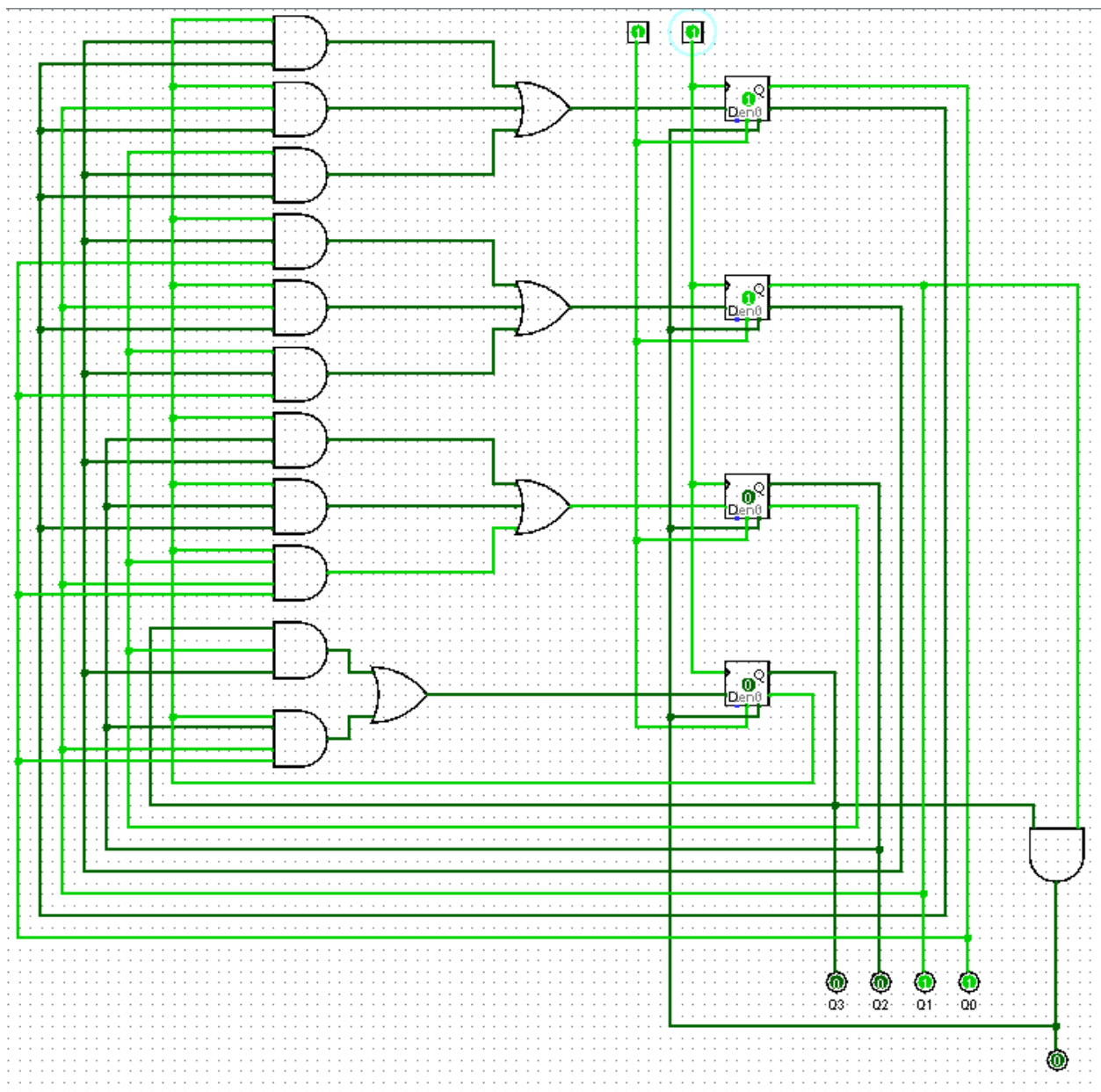


USTP IC DESIGN AND VERIFICATION
DIGITAL LOGIC DESIGN
WEEK 3


NAME: Ali Irfan

ROLL NO: 22FA-036-CE


1) MOD 10 Counter (0-9)




2) MOD 6 Counter (0-5)

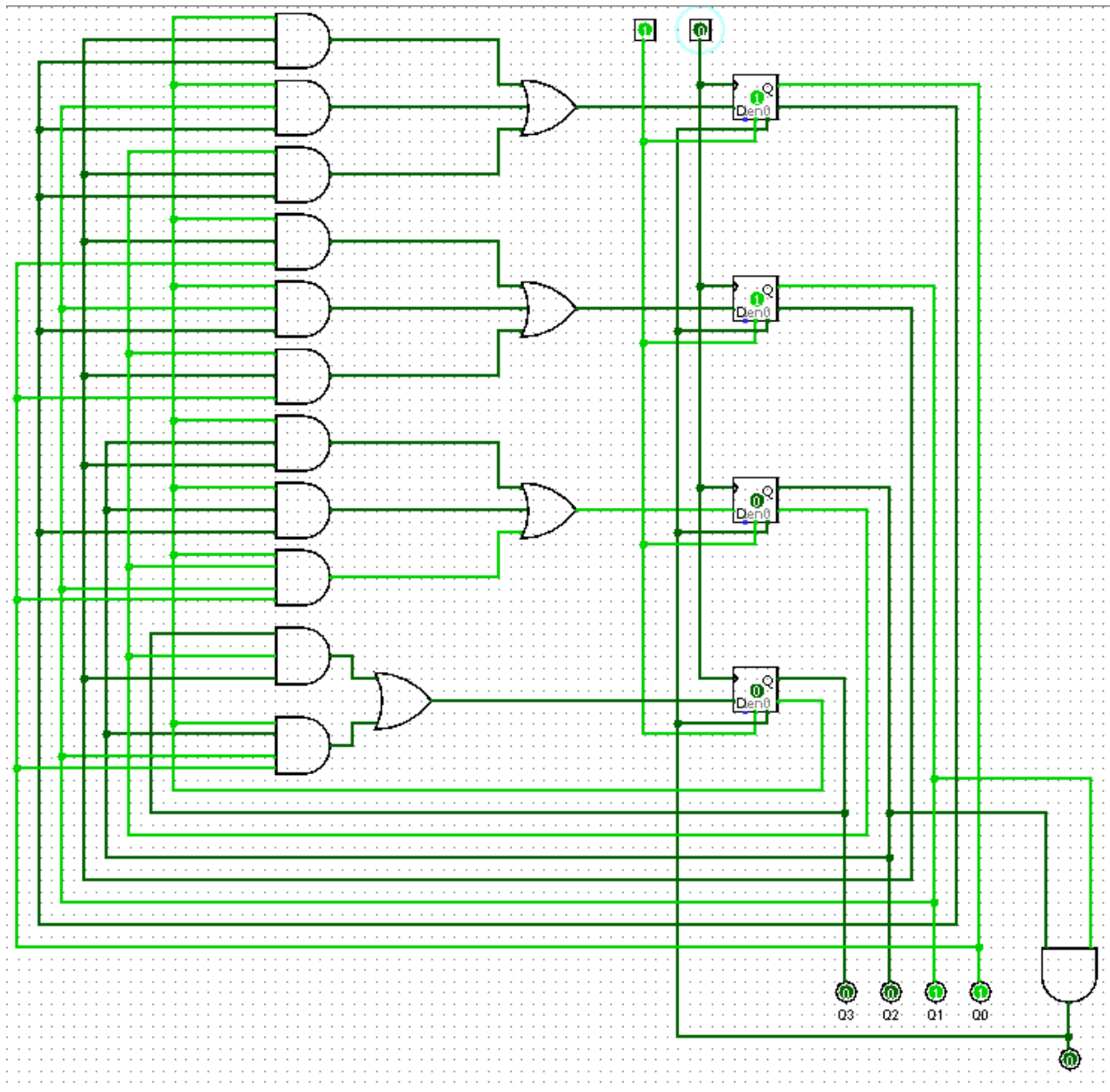


3) 3 Bit Grey Code Counter using JK

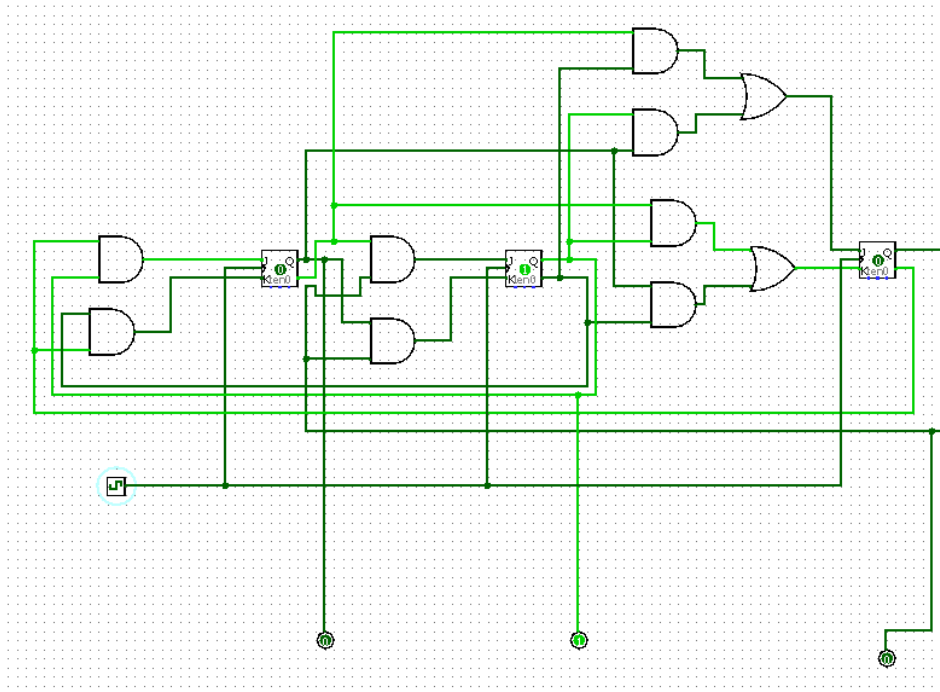


4) 3 Bit Grey Code Counter using D

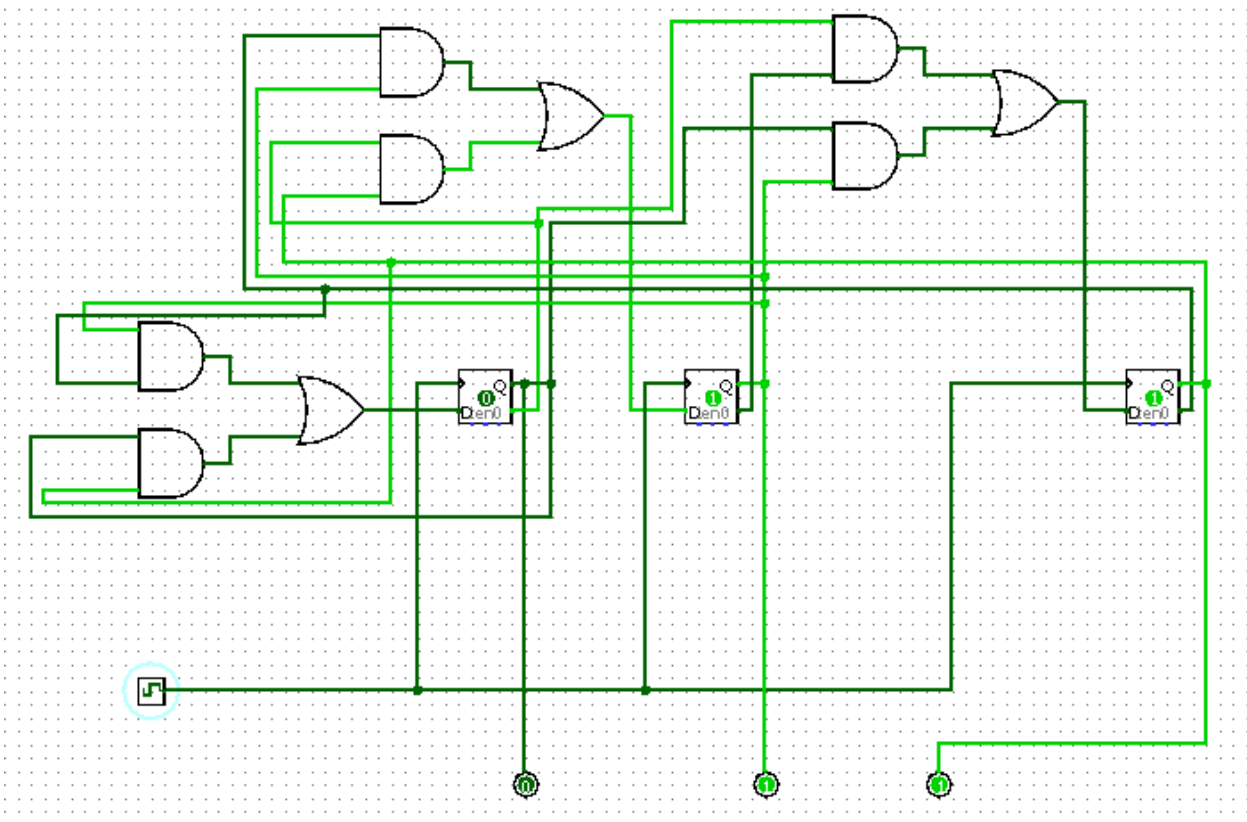


5) Mealy state machine example

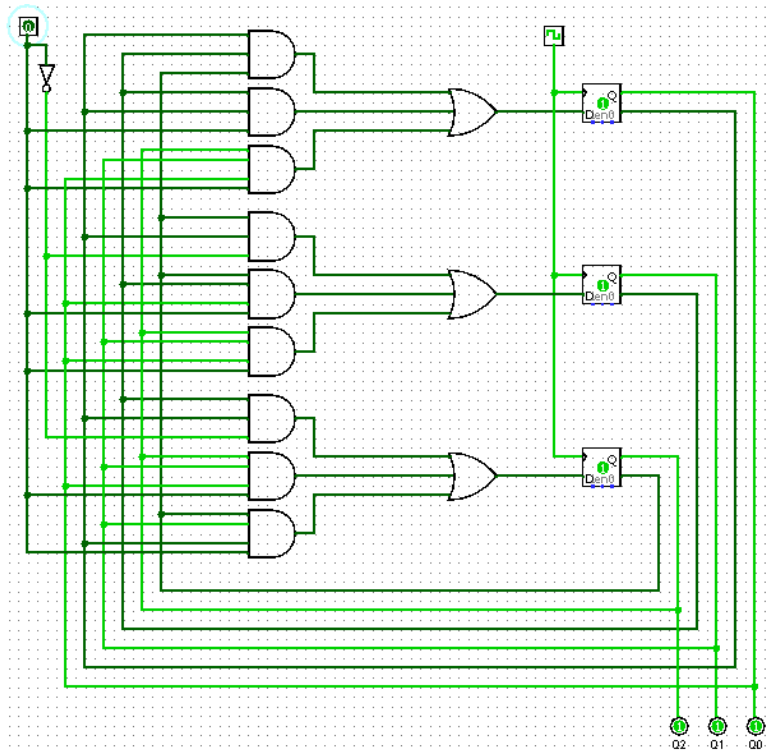


6) 4 Bit counter using JK

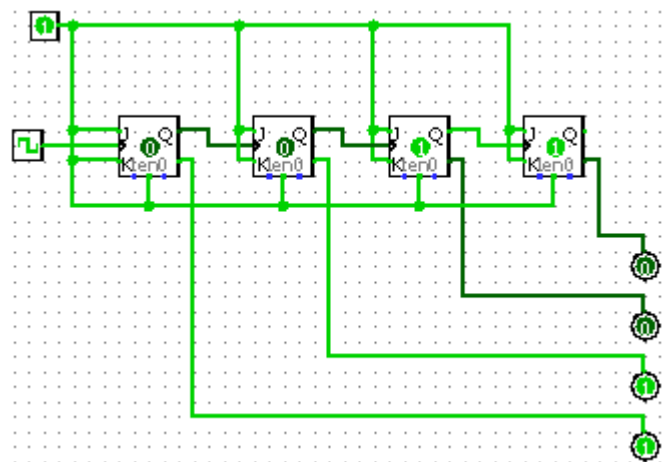


7) 3 Bit counter using JK

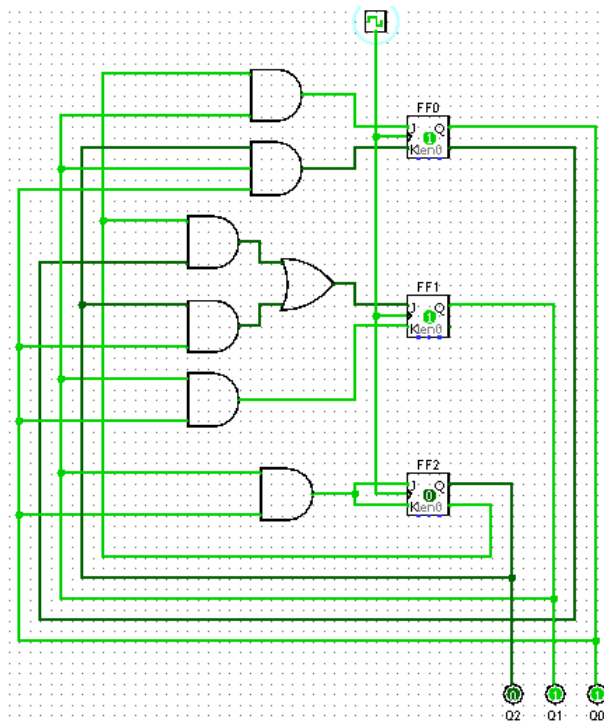


8) 3 Bit counter using D

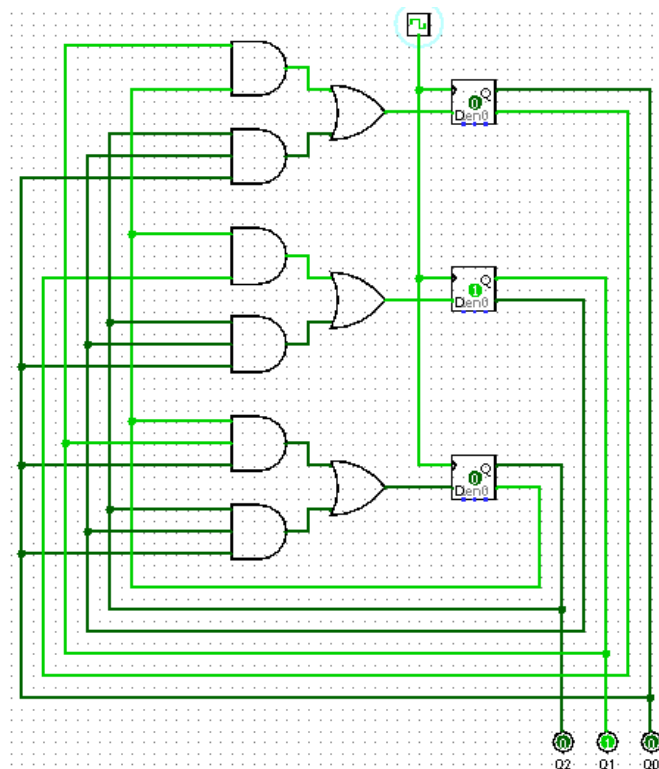


9) States example

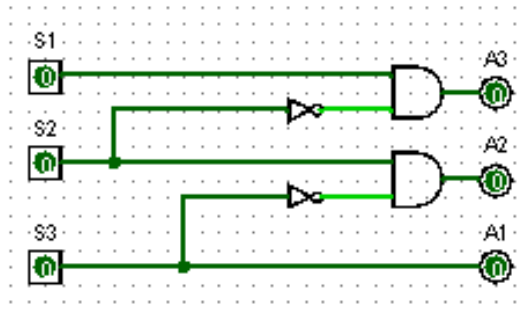


10) SISO

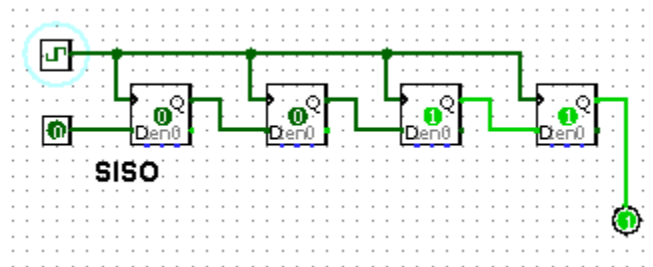


11) SIPO

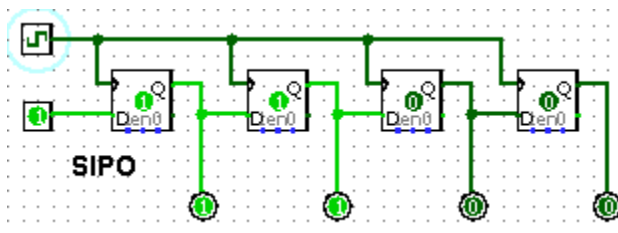


12) PISO

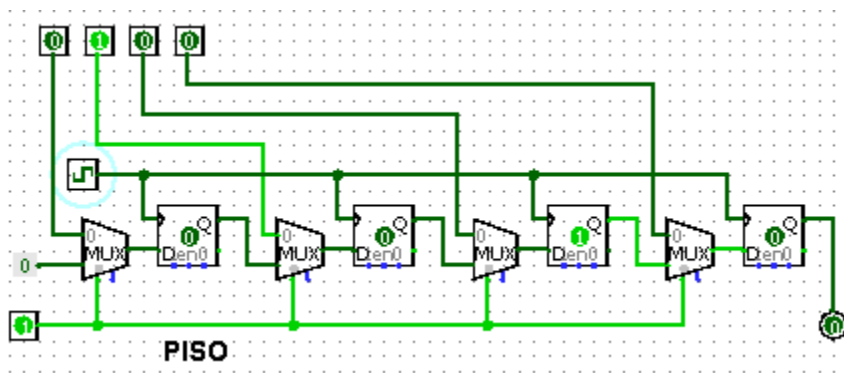


13) PIPO

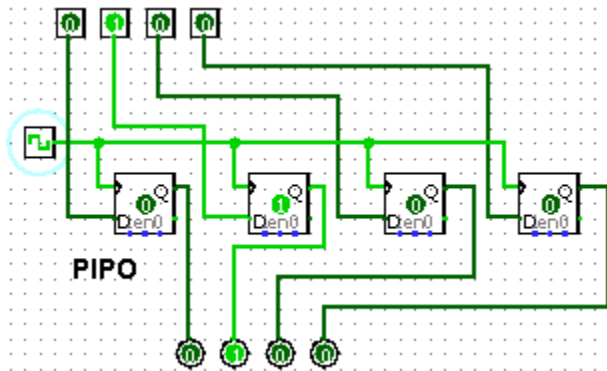


14) 8 Bit PIPO

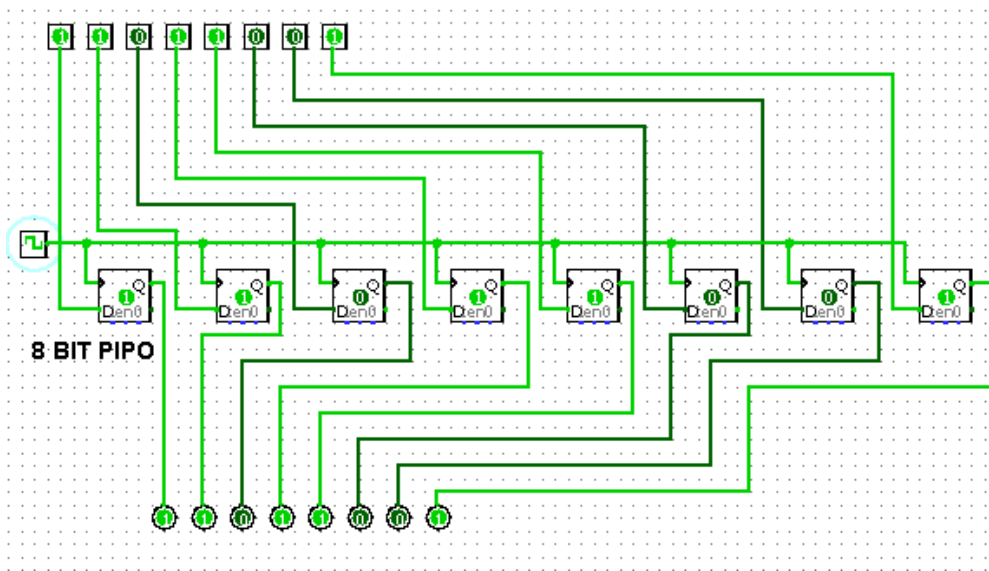


15) Circular shift register

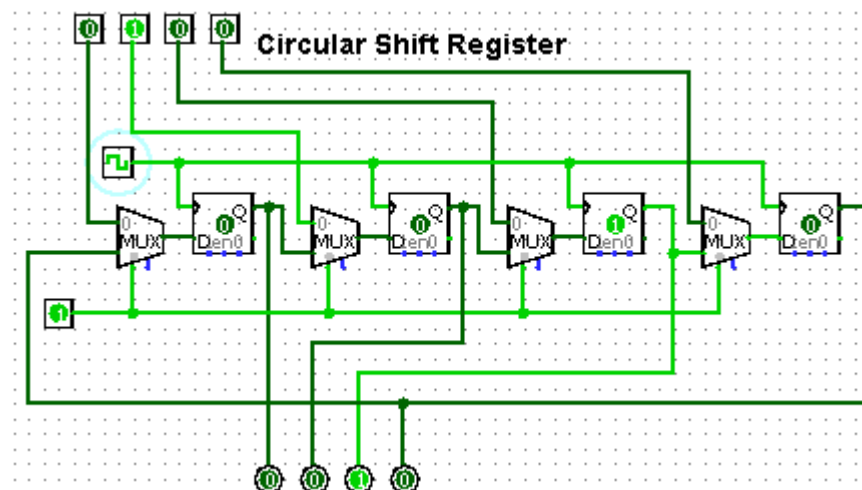


16) Ring Counter

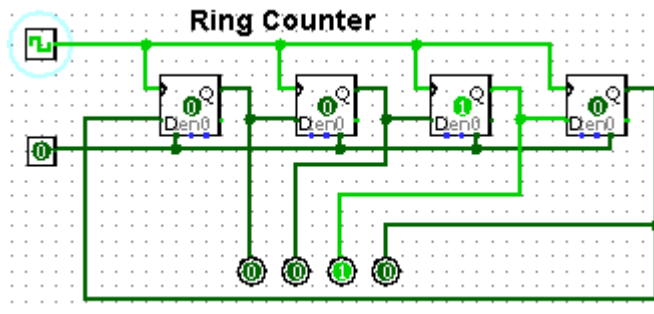


17) 5 Bit Ring counter

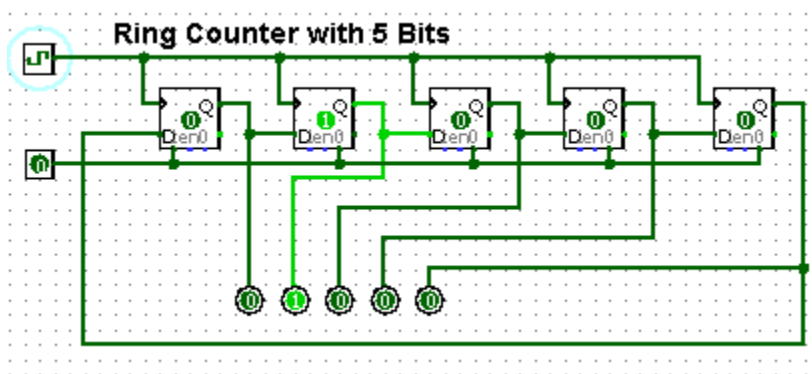

18) Johnson counter

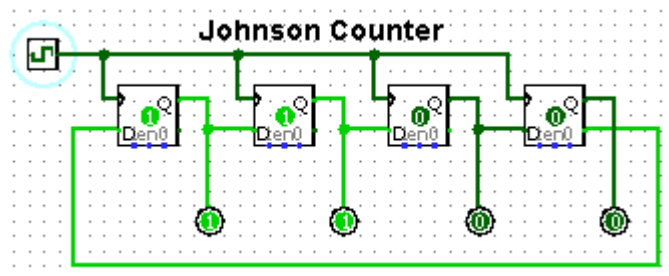

19) 5 Bit Johnson counter

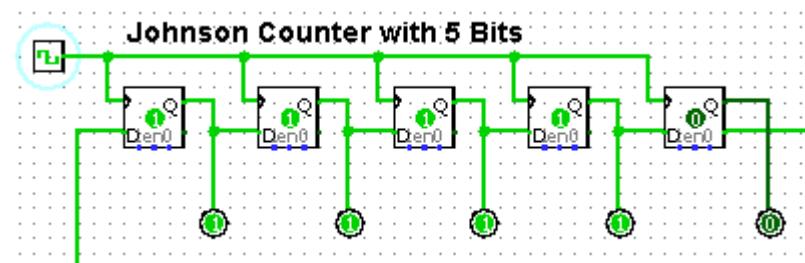

20) Circular shift register right/left both

